

S. No	Question	Blooms Taxonomy Level	Course Outcome
<b>UNIT -1</b>			
<b>INTRODUCTION TO ELECTRICAL ENGINEERING AND NETWORK ANALYSIS</b>			
1	<b>State</b> Kirchoff's voltage law and Kirchoff's current law?	Remember	2
2	<b>Explain</b> ideal voltage and current source?	Understand	1
3	<b>Discuss</b> the applications of both series and parallel combination?	Understand	2
4	<b>Discuss</b> resistor, capacitor, and inductor with relevant expression?	Understand	2
5	<b>Explain</b> the equations for resistors in equivalent delta. If the resistors $R_a$ , $R_b$ and $R_c$ are connected electrically in star?	Evaluate	2
6	<b>State</b> Ohm's law?	Evaluate	1
7	<b>State</b> Superposition Theorem?	Remember	3
8	<b>State</b> Thevenin's Theorem?	Remember	3
9	<b>State</b> Maximum power transfer theorem?	Remember	3
10	<b>Explain</b> difference between series and parallel resistive circuit ?	Understand	2
<b>UNIT - II</b>			
<b>ALTERNATING QUANTITIES</b>			
1	<b>Define</b> RMS Value?	Remember	7
2	<b>State</b> advantages of alternating quantities?	Understand	7
3	<b>Define</b> form factor?	Remember	7



S. No	Question	Blooms Taxonomy Level	Course Outcome
4	<b>Define</b> peak factor?	Remember	7
5	<b>Explain</b> significance of J factor?	Understand	7
6	<b>Define</b> average Value?	Remember	7
7	<b>Explain</b> polar form and rectangular form?	Understand	7
8	<b>Differentiate</b> ac and dc quantities?	Understand	7
9	<b>Define</b> time period and frequency?	Remember	7
10	<b>Define</b> cycle and waveform?	Remember	7
<b>UNIT – III</b>			
<b>TRANSFORMERS</b>			
1	<b>Define</b> transformation ratio?	Remember	5
2	<b>Explain</b> the purpose of laminating the core in a transformer?	Understand	5
3	<b>Explain</b> the emf equation of a transformer and define each term. ?	Remember	5
4	<b>Explain</b> does transformer draw any current when secondary is open? Why?	Understand	5
5	<b>Explain</b> mutual induction principle?	Understand	5
6	<b>Explain</b> why the transformer measured in KVA?	Understand	5
7	<b>Discuss</b> what are the parts are in parts in transformer?	Understand	5
8	<b>Explain</b> the equivalent circuit diagram of transformer?	Understand	5
9	<b>Define</b> voltage regulation of a transformer?	Remember	5
10	<b>Explain</b> difference between core and shell type transformers?	Understand	5
<b>UNIT – IV</b>			
<b>DC AND AC MACHINES</b>			
1	<b>State</b> Fleming’s Right Hand Rule?	Remember	5
2	<b>State</b> Fleming’s Left Hand Rule?	Remember	5
3	<b>Write</b> down the emf equation of a dc generator?	Understand	5
4	<b>Write</b> down the torque equation of a D.C motor?	Understand	5
5	<b>State</b> the function of commutator and brushes?	Remember	5
6	<b>Define</b> slip in induction motor?	Remember	6
7	<b>Write</b> expression for rotor current frequency?	Understand	6
8	<b>What</b> is principle operation of 3-phase induction motor?	Understand	6
9	<b>Explain</b> the slip-torque characteristics of 3-phase induction motor?	Understand	6
10	<b>State</b> two types of induction motors?	Understand	6
<b>UNIT – V</b>			
<b>BASIC INSTRUMENTS</b>			
1	<b>What</b> are the types of measuring instruments?	Understand	4
2	<b>Write</b> a short notes on moving iron instruments?	Understand	4
3	<b>Write</b> a short notes on moving iron instruments with attraction type?	Understand	4
4	<b>Write</b> a short notes on moving iron instruments with repulsion type?	Understand	4
5	<b>Define</b> i. air friction damping ii. fluid friction damping iii. eddy current damping ?	Remember	4
6	<b>Write</b> short notes on spring control mechanism?	Understand	4
7	<b>Write</b> short notes on gravity control?	Understand	4
8	<b>What</b> is mean by instrument? Different types of instrument	Understand	4
9	<b>Write</b> different types of torques?	Understand	4
10	<b>Write</b> short notes on controlling torque?	Understand	4







## PART – B (LONG ANSWER QUESTIONS)

S. No	Question	Blooms Taxonomy Level	Course Outcome
<b>UNIT -1</b>			
<b>INTRODUCTION TO ELECTRICAL ENGINEERING AND NETWORK ANALYSIS</b>			
1	<b>Explain</b> two capacitors are connected in series then $C_{eq} = (C_1 * C_2) / (C_1 + C_2)$ ?	Evaluate	1
2	<b>Explain</b> derivation of star-delta conversion equations?	Evaluate	2
3	<b>Explain</b> derivation of delta-star conversion equations?	Evaluate	2
4	<b>Explain</b> in detail the volt-ampere relationship of R, L and C elements with neat diagrams?	Understand	1
5	<b>Explain</b> about series and parallel networks of resistor?	Understand	1
6	<b>Explain</b> about series and parallel networks of inductor?	Understand	1
7	<b>Explain</b> classification of network elements?	Understand	1
8	<b>Explain</b> superposition theorem?	Remember	3
9	<b>Explain</b> Thevinin's theorem?	Remember	3
10	<b>Derive</b> the condition for maximum power transfer theorem?	Evaluate	3
<b>UNIT –II</b>			
<b>ALTERNATING QUANTITIES</b>			
1	<b>Explain</b> following terms: i) Impedance ii) admittance iii) susceptance iv) conductance v) Power factor ?	Remember	7
2	<b>Write</b> about series RL circuit?	Understand	7
3	<b>Write</b> about series RC circuit?	Understand	7
4	<b>Explain</b> behavior of RLC Series circuit ?	Understand	7
5	<b>Explain</b> i) rectangular form ii) polar form ?	Understand	7
6	<b>Explain</b> significance of J-Operator?	Understand	7
7	<b>Write</b> equations for RMS value, average value, form factor and peak factor?	Understand	7
8	<b>Discuss</b> what are the advantages of AC quantities?	Understand	7
9	<b>Explain</b> conversion from rectangular form to polar form?	Understand	7
10	<b>Explain</b> conversion from polar form to rectangular form?	Understand	7
<b>UNIT –III</b>			
<b>TRANSFORMERS</b>			
1	<b>Describe</b> the construction details of transformer?	Understand	5
2	<b>Explain</b> the principle of operation of transformer?	Understand	5
3	<b>Explain</b> the OC test of a single phase transformer?	Understand	5
4	<b>Explain</b> the losses in a Transformer?	Understand	5
5	<b>Obtain</b> the condition for maximum efficiency of a transformer?	Evaluate	5
6	<b>Obtain</b> the equivalent circuit of a single phase transformer?	Evaluate	5
7	<b>Explain</b> the SC test of a single phase transformer?	Understand	5
8	<b>Explain</b> the determination of deducing equivalent circuit parameters?	Understand	5
9	<b>Explain</b> the ON load condition of a transformer?	Understand	5
10	<b>Explain</b> the NO load condition of a transformer?	Understand	5
<b>UNIT –IV</b>			
<b>DC AND AC MACHINES</b>			
1	<b>Explain</b> the classification of DC generator?	Understand	5
2	<b>Derive</b> the equation for induced EMF of a DC generator?	Evaluate	5
3	<b>Derive</b> the torque equation of DC motor?	Evaluate	5
4	<b>Explain</b> the principle and construction of a 3 phase induction motor?	Understand	6

S. No	Question	Blooms Taxonomy Level	Course Outcome
5	<b>Derive</b> the expression for rotor frequency?	Evaluate	6
6	<b>Explain</b> why does an induction motor never runs at Synchronous speed?	Understand	6
7	<b>Obtain</b> the condition for maximum running torque of an induction motor?	Understand	6
8	<b>Explain</b> the classification of DC Motor and explain?	Understand	6
9	<b>Explain</b> the significance of back EMF in a DC motor?	Understand	6
10	<b>Explain</b> the load characteristics of shunt, series and compound generators?	Understand	6
<b>UNIT -V</b>			
<b>BASIC INSTRUMENTS</b>			
1	<b>Explain</b> working principle of permanent magnet moving coil instrument?	Understand	4
2	<b>Explain</b> working principle of moving iron repulsion type instrument?	Understand	4
3	<b>Explain</b> working principle of moving iron attraction type instrument?	Understand	4
4	<b>Explain</b> working of different types of torques produced in indicating instruments?	Understand	4
5	<b>Explain</b> i) Deflecting torque ii) Controlling torque iii) Damping torque?	Understand	4
6	<b>Mention</b> advantages and disadvantages of MI instruments?	Understand	4
7	<b>Explain</b> the essential requirements of instruments?	Understand	4
8	<b>Classify</b> of electrical instruments?		4
9	<b>Discuss</b> advantages and disadvantages of MI instruments?	Understand	4
10	<b>Explain</b> the significance of controlling torque and damping torque relevant to the operation of indicating instruments?	Understand	4

## PART - C (ANALYTICAL QUESTIONS)

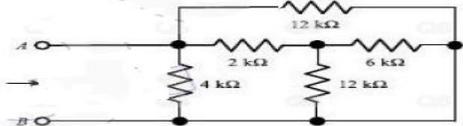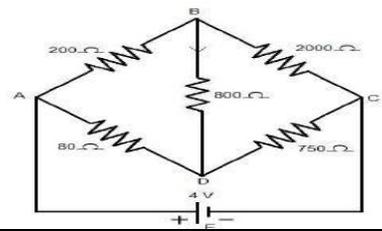S. No	Question	Blooms Taxonomy Level	Course Outcome
<b>UNIT -1</b>			
<b>INTRODUCTION TO ELECTRICAL ENGINEERING AND NETWORK ANALYSIS</b>			
1	<b>Find</b> the equivalent resistance for the following circuit? 	Apply	2
2	<b>Determine</b> the current through 800 ohm resistor in the network shown in figure 	Apply	2
3	If current flowing through a coil changes at the rate of 2amps/sec and the voltage induced is 20v. <b>Find</b> the inductance value?	Apply	1
4	By using Thevinin's theorem <b>Determine</b> the current through 5 ohm resistor?	Apply	3

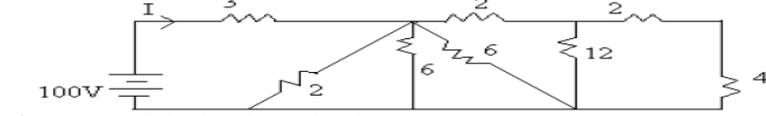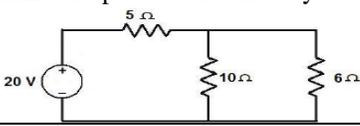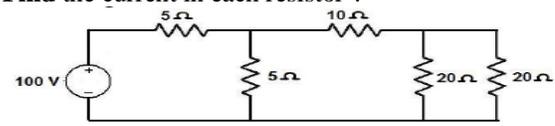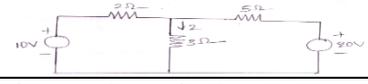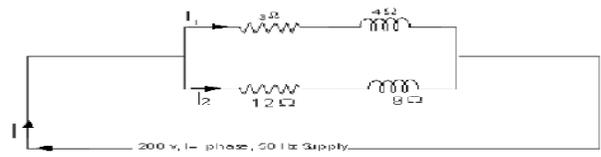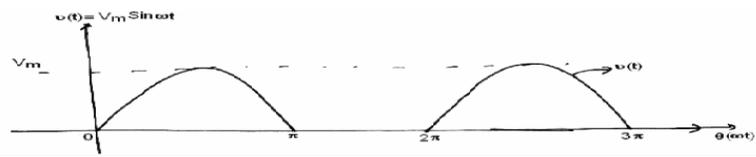S. No	Question	Blooms Taxonomy Level	Course Outcome
			
5	 <p><b>Find</b> current I in the above circuit?</p>	Apply	2
6	 <p><b>Find</b> the power consumed by each resistor?</p>	Apply	1
7	 <p><b>Find</b> the current in each resistor ?</p>	Apply	3
8	<p><b>Calculate</b> how to combine four 100 ohm resistors to obtain an equivalent resistance of a. 25 ohm, b. 60 ohm, c. 40 ohms?</p>	Apply	2
9	 <p><b>Calculate</b> the current 'I' shown in figure using super position theorem?</p>	Apply	2
10	<p>If 3 capacitors of values 2mF, 4mF, 5mF are connected in parallel. <b>Calculate</b> the effective capacitance?</p>	Apply	2
<b>UNIT – II</b>			
<b>ALTERNATING QUANTITIES</b>			
1	<p>A circuit consists of a resistance of 15ohm, a capacitance of 200 micro Farad and inductor of 0.05H all in series. If supply of 230V, 50Hz is applied to the ends of circuit. <b>Calculate</b> i) Current in the coil ii) Potential difference across each element?</p>	Apply	7
2	<p><b>Write</b> about series RC circuit?</p>	Understand	7
3	<p><b>Solve</b> the following parallel circuit and find out current in each branch and total current as shown in figure</p> 	Apply	7
4	<p><b>Calculate</b> the RMS, and average values of an alternating quantity given by <math>v = 20 \cos(314t)</math>?</p>	Apply	7
5	<p><b>Find</b> form factor and peak factor?</p> 	Apply	7

S. No	Question	Blooms Taxonomy Level	Course Outcome
6	<p><b>Determine</b> the average and effective values of saw-tooth waveform as shown in below figure</p>	Apply	7
7	Two impedances $z_1=20+j10$ and $Z_2= 10-j30$ are connected in parallel and this combination is connected in series with $Z_3=30+jx$ . <b>Find</b> the value of 'x' which will produce resonance?	Apply	7
8	<b>Convert</b> from rectangular to polar i) $z=30+j60$ ii) $z=45+j50$ ?	Apply	7
9	<p><b>Find</b> the input impedance of the circuit shown in figure(b) below .assume the circuit operates at <math>\omega=50\text{rad/sec}</math>?</p>	Apply	7
10	<b>Find</b> the voltage across RL phase angle in series R-L circuit, with $R = 100$ ohms and $L = 50\text{mH}$ and input voltage $10\text{V}$ , $100\text{Hz}$ ?	Apply	7
<b>UNIT – III</b>			
<b>TRANSFORMERS</b>			
1	A 125 KVA transformer having primary voltage of 2000V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses, <b>calculate</b> : i) The full load primary and secondary currents. ii) The no-load secondary induced emf. iii) Maximum flux in the core.	Apply	5
2	Open Circuit and short circuit tests on a single phase transformer gave the following results. $V_0=200\text{V}$ , $I_0=0.7\text{A}$ , $W_0=20\text{W}$ ----- test from primary side $V_S =10\text{V}$ , $I_S =10\text{A}$ , $W_S =40\text{W}$ ----- test from primary side. <b>Determine</b> the equivalent circuit referred to primary side?	Apply	5
3	A transformer supplied a load of 32A at 415V. If the primary voltage is 3320V, <b>find</b> the following: (a) Secondary volt ampere (b) Primary current (c) Primary volt ampere. Neglect losses and magnetizing current.	Apply	5
4	A single phase transformer has 50 primary and 1000 secondary turns. Net cross sectional area of the core is $500 \text{ cm}^2$ . If the primary winding is connected to 50 Hz supply at 400 V, <b>Calculate</b> the value of Maximum flux density on core and the emf induced in the secondary?	Apply	5
5	A transformer with 40 turns on the high voltage winding is used to step down the voltage from 240V to 120V. <b>Find</b> the number of turns in the low voltage winding. Open circuit and short circuit tests on a 5 KVA, 220/400V, 50 Hz, single phase transformer gave the following results: OC Test: 220V, 2A, 100W (lv side) SC Test: 40V, 11.4A, 200W ( hv side) Obtain the equivalent circuit?	Apply	5
6	A 3300/230V, 50Hz, 1-phase transformer is to be work at maximum flux density of $1.2 \text{ wb/m}^2$ in the core is $150 \text{ cm}^2$ . <b>Calculate</b> suitable value of primary and secondary turns?	Apply	5
7	A single phase 50Hz transformer has 80 turns on the primary winding and 280 in the secondary winding. The voltage applied across the primary winding is 240 V. <b>Calculate</b> (i) the maximum flux density in the core (ii) induced emf in the secondary winding. The net cross sectional area of the core can be taken $200\text{cm}^2$ ?	Apply	5

S. No	Question	Blooms Taxonomy Level	Course Outcome
8	A 15kVA 2400-240-V, 60 Hz transformer has a magnetic core of 50-cm <sup>2</sup> cross section and a mean length of 66.7 cm. The application of 2400 V causes magnetic field intensity of 450 AT/m (RMS) and a maximum flux density of 1.5 T. <b>Determine</b> i. The turn's ratio ii. The number of turns in each winding iii. The magnetizing current	Apply	5
9	The emf per turn of a 1- $\phi$ , 2200/220 V, 50 Hz transformer is approximately 12V. <b>Calculate</b> i) The number of primary and secondary turns, and ii) The net cross-sectional area of core for a maximum flux density of 1.5 T.	Apply	5
10	A 440/110 v transformer has a primary resistance of 0.03 ohms and secondary resistance of 0.02 ohms if iron losses at normal input is 150 watts. <b>Determine</b> the secondary current at which maximum efficiency will occur and the value of this maximum efficiency at a unity power factor load?	Apply	5
<b>UNIT –IV</b> <b>DC AND AC MACHINES</b>			
1	<b>Calculate</b> the e.m.f by 4 pole wave wound generator having 65 slots with 12 conductors per slot when driven at 1200 rpm the flux per pole is 0.02 wb?	Apply	5
2	A dynamo has a rated armature current at 250 amps what is the current per path of the armature if the armature winding is lap or wave wound? The machine has 12 poles.	Apply	5
3	A 6 pole lap wound dc generator has 600 conductors on its armature flux per pole is 0.02 wb. <b>Calculate</b> i. The speed at which the generator must be run to generate 300v. ii. What would be the speed if the generated were wave wound?	Apply	5
4	A 230 volts dc shunt motor takes 51 A at full load. Resistances of armature and field windings are 0.1ohm and 230 ohms respectively. <b>Determine</b> i. armature current ii. field current iii. back emf developed at full load?	Apply	5
5	In case of an 8-pole induction motor the supply frequency was 50 Hz and the shaft speed was 735 rpm. <b>Determine</b> i) Synchronous speed ii) Slip speed per unit slip iii) Percentage slip?	Apply	6
6	<b>Calculate</b> the value of torque established by the armature of a 4pole motor having 774 conductors, two paths in parallel, 24 m wb flux per pole , when the total armature current is 50 amps.	Apply	5
7	A 6 pole DC Long shunt generator having an armature ,series and shunt field resistances of 0.25 $\Omega$ ,0.5 and 100 $\Omega$ respectively delivers a load current of 35 Amps at a voltage of 200V.Take 2Volt as total brush drop. <b>Calculate</b> the induced EMF?	Apply	5
8	<b>Calculate</b> the induced EMF for a 6 pole DC Shunt generator having an armature and field Resistances of 0.25 $\Omega$ and 50 $\Omega$ respectively delivers a load current of 25 Amps at a voltage of 220V . Take 1Volt as total brush drop	Apply	5
9	A 6 – pole dc shunt generator with a wave – wound armature has 960 conductors. It runs at a speed of 500 rpm. A load of 20 $\Omega$ is connected to the generator at a terminal voltage of 240V.The armature and field resistances are 0.3 $\Omega$ and 240 $\Omega$ respectively. <b>Find</b> the armature current, the induced emf and flux per pole?	Apply	5
10	A 6-pole, 50Hz squirrel cage induction motor runs on load at a shaft speed of 970 rpm. <b>Calculate</b> i. Percentage slip	Apply	6

S. No	Question	Blooms Taxonomy Level	Course Outcome
	ii. The frequency of the induced current in the rotor?		
<b>UNIT –V</b>			
<b>BASIC INSTRUMENTS</b>			
1	A moving-coil instrument gives a full scale deflection. When the current is 40 mA and its resistance is 25. <b>Calculate</b> the value of the shunt to be connected in parallel with the meter to enable it to be used as an ammeter for measuring currents up to 50 A?	Apply	4
2	A moving-coil instrument having a resistance of 10 ohms, gives a full scale deflection. When the current is 8 mA. <b>Calculate</b> the value of the multiplier to be connected in series with the instrument so that it can be used as a voltmeter for measuring full scale deflection up to 100 V?	Apply	4
3	A moving-coil instrument gives full scale deflection. For a current of 10 mA. Neglecting the resistance of the instrument. <b>calculate</b> the approximate value of series resistance needed to enable the instrument to measure up to i. 20 V ii. 100V iii. 250 V?	Apply	4
4	A meter of resistance 50 ohms has a full scale deflection of 4 mA. <b>Determine</b> the value of shunt resistance required in order that full scale deflection should be (a) 15 mA (b) 20 A (c) 100 A?	Apply	4
5	A moving-coil instrument having a resistance of 20, gives a full scale deflection when the current is 5 mA. <b>Calculate</b> the value of the multiplier to be connected in series with the instrument so that it can be used as a voltmeter for measuring full scale deflection up to 200 V?	Apply	4
6	A moving-coil instrument has a full scale deflection of 20 mA and a resistance of 25. <b>Calculate</b> the values of resistance required to enable the instrument to be used (a) as a 0–10A ammeter and (b) as a 0–100 V voltmeter. State the mode of resistance connection in each case?	Apply	4
7	A PMMC instrument has a coil dimensions 15mm*12mm. the flux density in the air gap is 1.8 mWb/m*m and the spring constant 0.14micro N-m/rad. <b>Determine</b> the number of turns required to produce an angular deflection of 90degrees when a current of 5mA is flowing through the coil?	Apply	4
8	A PMMC instrument has a coil dimensions 18mm*16mm. the flux density in the air gap is 1.5 mWb/m*m and the spring constant 0.18micro N-m/rad. <b>Determine</b> the number of turns required to produce an angular deflection of 90degrees when a current of 3mA is flowing through the coil?	Apply	4