

## 1. Group - A (Short Answer Questions)

S.No	QUESTION	Blooms taxonomy level	Course Outcomes
<b>UNIT-I P-N JUNCTION DIODE</b>			
1	<b>Define</b> Electronics?	Remembering	1
2	<b>Explain</b> about forward bias of diode?	Understanding	1
3	<b>Explain</b> about reverse bias of diode?	Understanding	1
4	<b>Write</b> the applications of diode?	Comprehension	3
5	<b>Draw</b> the V-I characteristics of diode?	Comprehension	2
6	<b>List</b> the differences between ideal diode and practical diode?	Remembering	1
7	<b>Define</b> diffusion capacitance?	Knowledge	2
8	<b>Define</b> transition capacitance?	Remembering	2
9	<b>Define</b> static resistance?	Remembering	2
10	<b>Define</b> dynamic resistance	Remembering	2
11	<b>Explain</b> the load line analysis of diode?	Understanding	2
12	<b>Write</b> the equation of diode current	Remembering	2
13	<b>Define</b> Fermi level?	Remembering	1
14	<b>Sketch</b> V-I characteristics of a PN diode for the following conditions: $R_f = 0, R_r = 0, V_\gamma = 0$	Knowledge	2

S.No	QUESTION	Blooms taxonomy level	Course Outcomes
15	Sketch V-I characteristics of a PN diode for the following conditions: $R_F = 0, R_r = 0, V_\gamma = 0.6$	Comprehension	2
16	Define reverse saturation current?	Remembering	1
17	Define cut-in voltage?	Remembering	1
18	Write the differences between avalanche and zener breakdown mechanisms?	Knowledge	1
19	Define zener breakdown mechanism?	Remembering	1
20	Define depletion region?	Remembering	1
21	Explain the temperature dependence of VI characteristics of PN diode?	Understanding	1
22	Define doping?	Remembering	1
23	Explain about extrinsic semiconductor	Understanding	1
24	Explain about unbiased PN junction?	Understanding	1
25	Write down the expression for diode current?	Knowledge	1
26	Define drift current?	Remembering	1
27	List the applications of Zener diode?	Analyzing	1
28	Define forbidden energy gap?	Remembering	1
29	With appropriate circuit diagram explain the DC load line analysis of semiconductor diode?	Analysis	1
30	Define Peak Inverse voltage of a diode?	Remembering	1
31	What is the principle of operation of photodiode?	Knowledge	1
32	Give the principle of operation of Light Emitting Diode?	Analysis	1
33	Define diffusion current?	Remembering	1
34	List the applications of LED.	Analyzing	1
35	Draw the two transistor equivalent circuit of a SCR	Analysis	1
38	Define holding current in a SCR?	Remembering	1
39	Draw the V-I characteristics of SCR?	Analysis	2
40	Explain why a SCR is operated only in the forward biased condition?	Understanding	2
41	Explain how triggering of an SCR can be controlled by the gate signal supplied?		1
42	List the applications of varactor diode?	Analyzing	1
43	Define photodiode?	Remembering	
44	Define DIAC?	Remembering	1
45	Define TRIAC?	Remembering	1
<b>UNIT-II</b>			
<b>RECTIFIERS AND FILTERS</b>			
1	Define rectifier?	Remembering	3
2	Define ripple factor?.	Remembering	3
3	Compare the rectifier and regulator?	Comprehension	3
4	Define transformer utilization factor?	Remembering	3
5	Define efficiency?	Remembering	3
6	Define full wave rectifier?	Remembering	3

7	<b>What</b> are the merits of full wave rectifier?	Application	3
<b>S.No</b>	<b>QUESTION</b>	<b>Blooms taxonomy level</b>	<b>Course Outcomes</b>
8	<b>List</b> the disadvantages of full wave rectifier?	Analyzing	3
9	<b>Draw</b> the block diagram of shunt voltage regulator?	Knowledge	3
10	<b>Draw</b> the block diagram of series voltage regulator?	Knowledge	3
11	<b>Define</b> regulator?	Remembering	3
12	<b>Draw</b> the circuit diagram of half wave rectifier?	Synthesis	4
13	<b>Draw</b> the circuit diagram of full wave rectifier?	Evaluation	4
14	<b>Define</b> line regulation and load regulation?	Remembering	4
15	<b>Give</b> the advantages and disadvantages of HWR and FWR?	Knowledge	4
16	<b>What</b> is the need for a filter in rectifier?	Knowledge	4
17	What is the need for voltage regulators? What are the drawbacks of unregulated power supply?	Knowledge	4
18	<b>Draw</b> the circuit diagram of $\pi$ -section filter?		4
19	Explain about zener regulator?	Comprehension	4
20	Draw the circuit diagram of L-section filter?	Comprehension	4
<b>UNIT-III</b>			
<b>BIPOLAR JUNCTION TRANSISTOR AND UJT</b>			
1	Define Transistor?	Remembering	5
2	What is meant by operating point Q?	Comprehension	5
3	Draw the symbols of NPN and PNP transistor?	Comprehension	5
4	Explain the operation of BJT and its types?	Understanding	5
5	Explain the breakdown in transistor?	Understanding	5
6	Explain the transistor switching times?	Understanding	5
7	Define Transistor current?	Remembering	5
8	Define early effect or base width modulation?	Remembering	5
9	Explain about transistor amplifier?	Understanding	5
10	Define current amplification factor?	Remembering	5
11	When does a transistor act as a switch?	Comprehension	5
12	Explain about the various regions in a transistor?	Understanding	5
13	Draw the small signal model of a CE configuration?	Knowledge	6
14	Draw the output characteristics of NPN transistor in CE configuration?	Comprehension	6
15	Define $h_{ie}$ and $h_{fe}$ in CE configuration?	Remembering	6
16	Define $h_{oe}$ and $h_{re}$ in CB configuration?	Remembering	6
17	Define saturation region?	Remembering	6
18	Write the relation between $I_C$ , $\beta$ , $I_B$ and $I_{CBO}$ in a BJT?	Knowledge	6
19	Define cutoff region?	Remembering	6
20	Define active region?	Remembering	6
21	Describes the various current components in a BJT?	Knowledge	6
22	Define amplifier?	Remembering	6
23	Draw the hybrid model of a CB configuration?	Knowledge	6

24	Write a note on transistor construction?	Comprehension	6
<b>S.No</b>	<b>QUESTION</b>	<b>Blooms taxonomy level</b>	<b>Course Outcomes</b>
25	What are the differences between BJT and UJT?	Comprehension	6
26	Draw the equivalent circuit of a UJT	Comprehension	6
27	Draw the V-I characteristics of UJT?	Analyzing	6
28	What do you mean by regeneration in UJT?	Understanding	6
29	Explain the terms peak voltage and valley current in UJT?	Understanding	6
30	Write down applications of UJT?	Remembering	6
<b>UNIT-IV</b>			
<b>TRANSISTOR BIASING AND STABILIZATION</b>			
1	Define biasing?	Remembering	7
2	Why biasing is necessary in BJT amplifiers?	Knowledge	7
3	Define Q-point?	Remembering	7
4	Explain the concept of dc load line with the help of neat diagram?	Knowledge	7
5	Draw and explain the ac load line?	Evaluation	7
6	Define three stability factors?	Remembering	7
7	Which biasing method provides more stabilization amongst the three types of biasing methods?	Application	7
8	Compare the advantages and disadvantages of biasing schemes?	Knowledge	7
9	Draw the circuit diagram of a collector to base bias circuit of CE amplifier?	Evaluation	8
10	Write down advantages of fixed bias circuitry?	Comprehension	7
11	Draw the circuit diagram of a fixed bias circuit of CE amplifier?	Knowledge	8
12	Draw a circuit employing a sensistor compensation?	Application	8
13	Write down disadvantages of fixed bias circuit?	Application	8
14	Define thermal runaway?	Remembering	7
15	Define thermal resistance?	Remembering	7
16	Define stability factors $s'$ and $s''$ ?	Remembering	7
17	Define thermal stability	Remembering	7
18	Draw the circuit diagram of a self bias circuit of CE amplifier?	Analysis	8
19	Draw the circuit diagram of an emitter feedback bias circuit of CE amplifier?	Application	8
20	List out the different types of biasing methods?	Analyzing	8
21	A Ge transistor having $\beta=100$ and $V_{be}=0.2v$ is used in a fixed bias amplifier circuit where $v_{cc}=16v, R_c=5 K\Omega$ and $R_B= 790 K\Omega$ determine its operating point.	Analyzing	8
22	Differentiate bias stabilization and compensation techniques?	Evaluation	8
<b>UNIT-V</b>			
<b>Field Effect Transistor and FET Amplifiers</b>			
1	Why FET is called a voltage operated device?	Evaluation	9
2	List the important features of FET?	Knowledge	9

3	Draw the functional diagram of JFET?	Knowledge	9
<b>S.No</b>	<b>QUESTION</b>	<b>Bloomstaxonomy level</b>	<b>Course Outcomes</b>
4	Write short notes on millers theorem?	Knowledge	9
5	Give the classifications of FETs and their application areas?	Knowledge	9
6	Define pinch off voltage?	Comprehension	9
7	Draw the structure of an n-channel JFET?	Knowledge	9
8	Define rd and Gm?	Remembering	9
9	Draw the static characteristics curves of an n-channel JFET?	Comprehension	9
10	Draw the drain characteristics of depletion type MOFET?	Knowledge	9
11	Draw the small signal model of JFET?	Knowledge	9
12	Draw the transfer characteristics for P-channel JFET?	Comprehension	10
13	Draw the Drain V_I characteristics for p-channel JFET?	Knowledge	10
14	Explain about ohmic and saturation regions?	Understanding	10
15	Draw the drain characteristics of an n-channel enhancement type MOSFET?	Knowledge	10

## 2. Group - II (Long Answer Questions)

S.No	Question	Blooms taxonomy level	Course Outcomes
<b>UNIT-I</b>			
<b>P-N JUNCTION DIODE</b>			
1	<b>Define</b> Fermi level? By indicating the position of Fermi level in intrinsic, n-type and p- type semiconductor, explain its significance in semiconductors?	Remembering	1
2	<b>Distinguish</b> between drift and diffusion current in a semiconductor. State continuity equation?	Analyzing	1
3	Sketch the V-I characteristics of p-n junction diode for forward bias voltages. Distinguish between the incremental resistance and the apparent resistance of the diode?	Evaluation	2
4	<b>What</b> is potential energy barrier of the p-n junction? How does it arise and what is its order of magnitude?	Remembering	2
5	Explain the temperature dependence of VI characteristics of PN diode?	Comprehension	2
6	<b>Derive</b> an expression for total diode current starting from Boltzmann relationship in terms of the applied voltage?	Knowledge	2
7	<b>Explain</b> the V-I characteristics of Zener diode and distinguish between Avalanche and Zener Break downs?	Understanding	2
8	<b>Explain</b> in detail, the variation of following semiconductor parameters with temperature, i) Energy gap      ii) Conductivity.	Understanding	1
9	<b>Explain</b> the concept of diode capacitance. Derive expression for transition capacitance?	Understanding	1
10	<b>Define</b> depletion region at p-n junction? What is the effect of forward and reverse biasing of p-n junction on the depletion region? Explain with necessary diagrams?	Remembering	1
11	<b>Explain</b> Zener and avalanche breakdown mechanisms in detail?	Comprehension	1

S.No	Question	Blooms taxonomy level	Course Outcomes
12	<b>Differences</b> between 1.Static and dynamic resistances of a p – n diode. 2.Transition and Diffusion capacitances of a p – n diode	Distinguish	2
13	<b>Difference</b> between 1.Volt – Ampere characteristics of a single silicon p – n diode and two indetical silicon p- n diodes connected in parallel. 2.Avalanch and zener break down mechanisms	Distinguish	2
14	<b>Explain</b> the tunneling phenomenon. Explain the characteristics of tunnel diode with the help of necessary energy band diagrams?	Understanding	2
15	<b>What</b> is the photo diode? Explain its principle of operation and applications in detail?	Remembering	2
16	<b>Explain</b> the construction and working of photo diode?	Understanding	2
17	<b>Explain</b> about : i) Varactor diode ii) Schottky Barrier diode With necessary sketches.	Understanding [7+8]	2
18	Sketch the static characteristics and firing characteristics of SCR and explain the shape of the curve?		2
19	<b>Explain</b> Schottky diode with necessary sketches?	Understanding	2
20	<b>Explain</b> how a variable capacitance can be built using a varactor diode?	Understanding	2
21	<b>Define</b> the following terms for a PN diode 1. Dynamic resistance      2.Load line. 3. Difference capacitance.    4. Reverse saturation current.	Remembering	2
<b>UNIT-II</b> <b>RECTIFIERS AND FILTERS</b>			
1	Draw the block diagram of a regulated power supply and explain its operation?	Understanding	3
2	Draw the circuit of a half-wave-rectifier and find out the ripple factor, % regulation? Efficiency and PIV?	Analyzing	4
3	Draw the circuit of bridge rectifier and explain its operation with the help of input and output waveforms?	Analyzing	4
4	<b>With</b> suitable diagrams, <b>explain</b> the working of centre-tapped full wave rectifier. Derive expressions for $V_{DC}$ , $I_{DC}$ , $V_{rms}$ and $I_{rms}$ for it?	Understanding	4
5	<b>Explain</b> the relative merits and demerits of all the rectifiers?	Understanding	3
6	<b>Compare</b> the performance of Inductor filter and capacitor filter?	Understanding	3
7	<b>Derive</b> the expression for the ripple factor of $\pi$ -Section filter when used with a Half-wave-rectifier. Make necessary approximations?	Analyzing	4
8	<b>Derive</b> the expression for the ripple factor of $\pi$ -Section filter when used with a Full-wave-rectifier. Make necessary approximations?	Analyzing	4
9	<b>Define</b> Ripple factor and form factor. Establish a relation between them?	Remembering	3
10	<b>Explain</b> the necessity of a bleeder resistor in an L – section filter used with a Full Wave filter?	Understanding	4
11	<b>List</b> out the merits and demerits of Bridge type Full Wave rectifiers over centre tapped type Full Wave rectifiers?	Analyzing	3
12	<b>Explain</b> about multiple L-section and multiple $\pi$ -section filters?	Understanding	4
13	<b>Compare</b> the performance of series inductor, L-section and $\pi$ -section filters?	Understanding	4


14	<b>Explain</b> the operation of inductor filter and derive expression for ripple factor?(FWR)	Understanding	4
<b>S.No</b>	<b>Question</b>	<b>Blooms taxonomy level</b>	<b>Course Outcomes</b>
15	<b>Explain</b> the operation of L-section filter and derive expression for ripple factor?(FWR)	Understanding	4
<b>UNIT-III</b>			
<b>BIPOLAR JUNCTION TRANSISTOR AND UJT</b>			
1	With a neat diagram <b>explain</b> the various current components in an NPN bipolar junction transistor & hence derive general equation for collector current, $I_c$ ?	Understanding	5
2	<b>Define</b> Early-effect; explain why it is called as base-width modulation? Discuss its consequences in transistors in detail?	Remembering	5
3	<b>How</b> transistor acts as an amplifier?	Remembering	6
4	<b>Draw</b> the input and output characteristics of a transistor in common emitter configurations?	Comprehension	6
5	<b>Draw</b> the input and output characteristics of a transistor in common base configurations?	Evaluation	6
6	<b>Draw</b> the input and output characteristic of a transistor in common collector configurations?	Comprehension	6
7	<b>Explain</b> the constructional details of Bipolar Junction Transistor?	Understanding	6
8	<b>Derive</b> the relation among $\alpha$ , $\beta$ and $\gamma$ ?	Evaluation	6
9	<b>What</b> is thermal runaway in transistors? Obtain the condition for thermal stability in transistors?	Remembering	6
10	<b>Describe</b> the significance of the terms, ' $\alpha$ ' and ' $\beta$ '. Establish a relation between them?	Evaluation	6
11	<b>Explain</b> how the UJT can be used as a negative-resistance device with the aid of static characteristics?	Understanding	6
12	<b>Give</b> the construction details of UJT & <b>explain</b> its operation with the help of equivalent circuits?	Understanding	6
13	<b>Explain</b> any two construction techniques of construction of transistor?	Understanding	6
14	<b>Explain</b> the application of a UJT as a relaxation oscillator?	Comprehension	6
15	With reference to bipolar junction transistors, <b>define</b> the following terms and explain. i) Emitter efficiency. ii) Base Transportation factor. iii) Large signal current gain.	Comprehension	6
<b>UNIT-IV</b>			
<b>TRANSISTOR BIASING AND STABILIZATION</b>			
1	<b>Define</b> biasing? Draw the fixed bias circuit and obtain the expression for the stability factor?	Remembering	8
2	<b>Draw</b> the collector-emitter feedback bias circuit and obtain the expression for the stability factor?	Comprehension	8
3	<b>Draw</b> the self bias circuit and obtain the expression for the stability factor. Discuss the advantages and disadvantages of self biasing?	Knowledge	8
4	<b>Draw</b> the emitter feedback bias circuit and obtain the expression for the stability factor?	Comprehension	8
5	<b>Define</b> 'Thermal Runaway' in transistors? Derive the condition to	Remembering	8


[9+6]

S.No	Question	Blooms taxonomy level	Course Outcomes
	prevent 'Thermal Runaway' in Bipolar Junction Transistors?		
6	<b>Draw</b> the circuit diagram & small signal equivalent of CB amplifier using accurate h-parameter model. Derive expressions for $A_v$ , $A_i$ , $R_i$ and $R_o$ ?	Application	7
7	<b>Draw</b> the circuit diagram of CC amplifier using hybrid parameters and derive expressions for $A_i$ , $A_v$ , $R_i$ , $R_o$ ?	Application	8
8	<b>What</b> are the compensation techniques used for $V_{BE}$ and $I_{CO}$ . Explain with help of suitable circuits?	Remembering	8
9	<b>Define</b> the stability factors with respect to the changes in $I_{CO}$ , $V_{BE}$ and $\beta$ . Why is the stability with respect to changes in $V_{CE}$ not considered?	Remembering	8
10	<b>Justify</b> statement "Potential divider bias is the most commonly used biasing method" for BJT circuits. Explain how bias compensation can be done in such biasing through diodes?	Evaluating	7
11	<b>Determine</b> the significance of operating point, DC and AC load lines to ensure active region operation of a BJT in CE amplifier application?	Evaluating	8
<b>UNIT-V</b>			
<b>Field Effect Transistor and FET Amplifiers</b>			
1	<b>Explain</b> the operation of FET with its characteristics and explain the different regions in transfer characteristics?	Comprehension	9
2	<b>Define</b> pinch-off voltage and trans conductance in field effect transistors?	Comprehension	9
3	With the help of neat sketches and characteristic curves <b>explain</b> the construction & operation of a JFET and mark the regions of operation on the characteristics?	Application	9
4	<b>Explain</b> how a FET can be made to act as a switch?	Knowledge	9
5	Bring out the differences between BJT and FET. <b>Compare</b> the three configurations of JFET amplifiers?	Knowledge	9
6	<b>Create</b> a relation between the three JFET parameters, $\mu$ , $r_d$ and $g_m$ ?	Creating	10
7	<b>How</b> a FET can be used as a voltage variable Resistance (VVR)?	Remembering	10
8	<b>Explain</b> the construction & operation of a P-channel MOSFET in enhancement and depletion modes with the help of static drain characteristics and transfer characteristics?	Understanding	9
9	<b>Sketch</b> the drain characteristics of MOSFET for different values of $V_{GS}$ & mark different regions of operation.	Comprehension	9
10	<b>Explain</b> the principle of CS amplifier with the help of circuit diagram. Derive the expressions for $A_v$ , input impedance and output Impedance?	Understanding	10
11	<b>Write</b> the expressions for mid-frequency gain of a FET Common Source?	Knowledge	9
12	Discuss the high frequency response of CD Configuration?	Knowledge	9
13	<b>What</b> is the effect of external source resistance on the voltage gain of a common source amplifier? Explain with necessary derivations?	Remembering	10
14	<b>Draw</b> the small-signal model of common drain FET amplifier. Derive expressions for voltage gain and output resistance?	Analyzing	10
15	<b>Draw</b> the small-signal model of common source FET amplifier.	Analyzing	10


S.No	QUESTION	Blooms taxonomy level	Course Outcomes
	Derive expressions for voltage gain and output resistance?		
16	<b>Draw</b> the small-signal model of common gate FET amplifier. Derive expressions for voltage gain and output resistance?	Analyzing	10
17	<b>List</b> any four merits of MOSFET to show that they are more suitable than JFETS in Integrated circuits?	Remembering	9
18	<b>Compare</b> enhancement and depletion modes of a MOSFET with the help of its characteristics and construction?	Analyzing	10
19	With a neat schematic, <b>explain</b> how amplification takes place in a common drain amplifier?	Understanding	10
20	<b>Explain</b> the significance of threshold voltage of a MOSFET. Discuss the methods to reduce threshold voltage, $V_T$ ?	Understanding	10
21	Derive the expression for transconductance of MOSFET?	Analyzing	10



### 3. Group - III (problems):

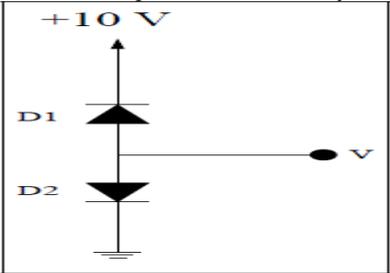
S.No	QUESTION	Blooms taxonomy level	Course Outcomes
<b>UNIT-I</b>			
<b>P-N JUNCTION DIODE</b>			
1		Application	2
2	<b>Find</b> the value of D.C. resistance and A.C resistance of a Germanium junction diode at 25° C with reverse saturation current, $I_o = 25\mu\text{A}$ and at an applied voltage of 0.2V across the diode?	Analysis	2
3	The reverse saturation current of a silicon p – n junction diode at an operating temperature of 27°C is 50 nA. <b>Estimate</b> the dynamic forward and reverse resistances of the diode for applied voltages of 0.8 V and - 0.4 V respectively?	Evaluating	2
4	The circuit shown in Figure (3.2) uses identical diodes for which $I_D = 1 \text{ mA}$ at $V_D = 0.7 \text{ V}$ with $n = 1$ . At 20°C, voltage V is measured by a very high resistance meter to be 0.1 V. By what factor does the reverse leakage current of these diodes exceed $I_s$ ? <b>Estimate</b> the value of V when the temperature is raised by 50°C.	Evaluating	2
			
5	A P-N junction germanium diode has a reverse saturation current of 0.10 $\mu\text{A}$ at the room temperature of 27°C.It is observed to be 30 $\mu\text{A}$ ,when the room temperature is increased. <b>Evaluate</b> the room temperature?	Evaluating	2
6	<b>Find</b> the factor by which the reverse saturation current of a silicon diode will get multiplied when the temperature is increased from 27° C to 82°C?	Remembering	2
7	<b>Determine</b> the values of forward current in the case of P-N junction diode, with $I_0=10 \mu\text{A}$ $V_f=0.8\text{V}$ at $T=300^\circ\text{K}$ .Assume silicon diode?	Evaluating	2
8	A p-n junction diode has a reverse saturation current of 30 $\mu\text{A}$ at a temperature of 125° C. At the same temperature, <b>find</b> the dynamic resistance for 0.2 V bias in forward and reverse direction?	Remembering	2
9	The voltage across a silicon diode at room temperature of 300°K is 0.7 V when 2 ma current flows through it. If the voltage increases to 0.75 v, <b>Evaluate</b> the diode current assuming $V_T=26\text{mv}$ .	Evaluating	2
10	<b>Determine</b> the dynamic forward and reverse resistance of p-n junction silicon diode when the applied voltage is 0.25 V at $T=3000\text{K}$ with give $I_0=2 \mu\text{A}$ ?	Evaluating	2
<b>UNIT –II</b>			
<b>RECTIFIERS AND FILTERS</b>			
1	A full wave bridge rectifier having load resistance of 100 $\Omega$ is fed with 220V, 50Hz through a step-down transformer of turns ratio 11:1. Assuming the diodes ideal, <b>find</b> DC output voltage Peak inverse voltage	Evaluating	4

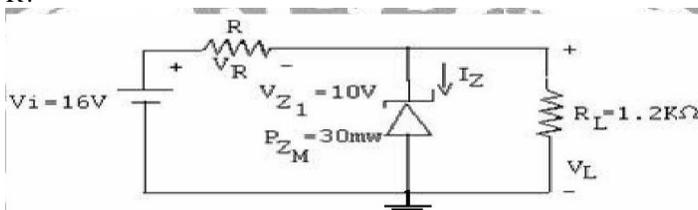	iii) Rectifier efficiency.		[9+6]
S.No	QUESTION	Blooms taxonomy level	Course Outcomes
2	<b>Determine</b> the ripple factor of an L-section filter comprising a 10H choke and 8 $\mu$ F capacitor, used with a FWR. The DC voltage at the load is 50V. Assume the line frequency as 50Hz?	Evaluating	4
			4
3	A bridge rectifier uses four identical diodes having forward resistance of 5 $\Omega$ each. Transformer secondary resistance is 5 ohms and the secondary voltage is 30V (rms). <b>Determine</b> the dc output voltage for $I_{dc} = 200$ mA and value of the output ripple voltage?	Evaluating	4
4	A 230 V, 60Hz voltage is applied to the primary of a 5:1 step down, center tapped transformer used in a full wave rectifier having a load of 900 $\Omega$ . If the diode resistance and the secondary coil resistance together have a resistance of 100 $\Omega$ , <b>determine</b> i) DC voltage across the load. ii) DC current flowing through the load. iii) DC power delivered to the load. iv) PIV across each diode.	Evaluating	4
			[8+7]
5	A HWR circuit supplies 100mA DC current to a 250 $\Omega$ load. <b>Find</b> the DC output voltage, PIV rating of a diode and the r.m.s. voltage for the transformer supplying the rectifier?	Evaluating	4
6	A full wave rectifier circuit uses two silicon diodes with a forward resistance of 20 $\Omega$ each. A DC voltmeter connected across the load of 1K $\Omega$ reads 55.4 volts. <b>Calculate</b> i) $I_{rms}$ ii) Average voltage across each diode iii) ripple factor iv) Transformer secondary voltage rating.	Evaluating	4
			[7+8]
7	<b>What</b> is the ripple factor if a power supply of 220 V, 50 Hz is to be Full Wave rectified and filtered with a 220 $\mu$ F capacitor before delivering to a resistive load of 120 $\Omega$ ? Compute the value of the capacitor for the ripple factor to be less than 15%.	Remembering	4
8	For the Zener diode circuit shown in Figure.1, <b>determine</b> $V_L$ , $V_R$ , $I_Z$ & R? 	Evaluating	4
9	In a Zener diode regulator, the supply voltage = 300V, $V_z = 220$ V, $I_z = 15$ mA and load current = 25mA. <b>Determine</b> the value of resistor required to be connected in series with the Zener diode?	Evaluating	4
10	A bridge rectifier uses four identical diodes having forward resistance of 5 $\Omega$ each. Transformer secondary resistance is 5 $\Omega$ and the secondary voltage of 30V(rms). <b>Determine</b> the dc output voltage for $I_{DC}=200$ mA	Evaluating	4

	and the value of the ripple voltage.		
S.No	QUESTION	Blooms taxonomy level	Course Outcomes
<b>A UNIT-III</b>			
<b>BIPOLAR JUNCTION TRANSISTOR AND UJT</b>			
1	<b>Determine</b> the values of $I_C$ and $I_E$ for a transistor with $\alpha_{dc} = 0.99$ and $I_{CBO} = 5\mu A$ , if $I_B$ is measured as $20\mu A$ ?	Evaluating	6
2	<b>Determine</b> the collector current and emitter current for a transistor with $\alpha = 0.99$ and $I_{CBO} = 490\mu A$ when the base current is $19\mu A$ ?	Evaluating	6
3	The reverse leakage current of the transistor when connected in CB configuration is $0.2\mu A$ while it is $18\mu A$ when the same transistor is connected in CE configuration. <b>Determine</b> $\alpha$ and $\beta$ of the transistor?	Evaluating	6
4	For an NPN transistor with $\alpha_N = 0.98$ , $J_{CO} = 2\mu A$ and $I_{EO} = 1.6\mu A$ connected in Common Emitter Configuration, <b>Determine</b> the minimum base current for which the transistor enters into saturation region. $V_{CC}$ and load resistance are given as $12V$ and $4.0K\Omega$ respectively?	Evaluating	6
5	If the base current in a transistor is $20\mu A$ when the emitter current is $6.4mA$ , what are the values of $\alpha_{dc}$ and $\beta_{dc}$ ? Also <b>determine</b> the collector current?	Evaluating	6
6	In a certain transistor, the emitter current is 1.02 times as large as the collector current. If the emitter current is $12mA$ , <b>find</b> the base current?	Evaluating	6
7	<b>A) Find</b> $\alpha_{dc}$ for each of the following values of $\beta_{dc} = 50$ and $190$ . <b>B) Find</b> $\beta_{dc}$ for each of the following values of $\alpha_{dc} = 0.995$ and $0.9765$	Evaluating	6
8	In a certain transistor, the emitter current is 1.09 times as large as the collector current. If the emitter current is $10mA$ , <b>find</b> the base current?	Evaluating	6
<b>UNIT-IV</b>			
<b>TRANSISTOR BIASING AND STABILIZATION</b>			
1	<b>Design</b> a collector to base bias circuit using silicon transistor to achieve a stability factor of 20, with the following specifications: $V_{CC} = 16V$ , $V_{BE} = 0.7V$ , $V_{CEQ} = 8V$ , $I_{CQ} = 4mA$ & $\beta = 50$ ?	Creating	8
2	<b>Draw</b> small signal equivalent circuit of Emitter Follower using accurate h-parameter model. For the emitter follower circuit with $R_S = 0.5K$ and $R_L = 5K$ , calculate $R_i$ , $A_V$ and $R_O$ . Assume, $h_{fe} = 50$ , $h_{ie} = 1K$ , $h_{oe} = 25\mu A/V$ .		8
3	A silicon NPN transistor has $I_{co} = 20nA$ and $\beta = 150$ , $V_{be} = 0.7V$ . It is operated in Common Emitter configuration having $V_{bb} = 4.5V$ , $R_b = 150K$ , $R_c = 3K$ , $V_{cc} = 12V$ . Find the emitter, base and collector currents and also verify in which region does the transistor operate. <b>What</b> will happen if the value of the collector resistance is increased to very high values?	Remembering	8
4	<b>Design</b> a self bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications: $V_{CC} = 16V$ , $V_{BE} = 0.7V$ , $V_{CEQ} = 8V$ , $I_{CQ} = 4mA$ & $\beta = 50$ ?	Creating	8
5	A bipolar junction transistor with $h_{ie} = 1100\Omega$ , $h_{fe} = 50$ , $h_{re} = 2.4 \times 10^{-4}$ , $h_{oe} = 25\mu A/V$ , is to drive a load of $1K\Omega$ in Emitter-Follower arrangement. <b>Estimate</b> $A_V$ , $A_I$ , $R_i$ & $R_o$ ?	Evaluating	8
6	<b>Design</b> an Emitter bias circuit using silicon transistor to achieve a stability factor of 20, with the following specifications: $V_{CC} = 16V$ , $V_{BE} = 0.7V$ , $V_{CEQ} = 8V$ , $I_{CQ} = 4mA$ & $\beta = 50$ .	Creating	8

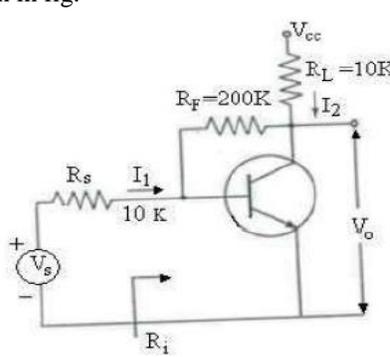S.No	QUESTION	Blooms taxonomy level	Course Outcomes
7	A bipolar junction transistor with $h_{ie} = 1100\Omega$ , $h_{fe} = 50$ , $h_{re} = 2.4 \times 10^{-4}$ , $h_{oe} = 25 \mu A/V$ , is to drive a load of $1K\Omega$ in CB amplifier arrangement. <b>Estimate</b> $A_v$ , $A_i$ , $R_i$ & $R_o$ ?	Evaluating	8
8	<b>Design</b> a fixed bias circuit using silicon transistor, with the following specifications: $V_{CC} = 16V$ , $V_{BE} = 0.7V$ , $V_{CEQ} = 8V$ , $I_{CQ} = 4 mA$ & $\beta = 50$ ?	Evaluating	8
9	<b>Design</b> a self bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications: $V_{CC} = 16V$ , $V_{BE} = 0.7V$ , $V_{CEQ} = 8V$ , $I_{CQ} = 4 mA$ & $\beta = 50$ ?	Evaluating	8
10	<b>Design</b> a self bias circuit for the following specifications: $V_{CC} = 12 V$ ; $V_{CE} = 2V$ ; $I_C = 4mA$ ; $h_{fe} = 80$ . Assume any other design parameters required. Draw the designed circuit.	Evaluating	8
11	<b>Compute</b> current gain, voltage gain, input and output impedance of the CB amplifier if it is driven by a voltage source of internal resistance $R_s=1k$ . The load impedance is $R_L=1K$ . The transistor parameters are $h_{ib}= 22$ , $h_{fb}= -0.98$ , $h_{rb}=2.9 \times 10^{-4}$ , $h_{ob}= 0.5 \mu A/V$ .	Analysis	8
12	<b>Determine</b> $A_i$ , $A_v$ , $R_i$ , $R_o$ of a transistor with $h_{ie}=1.1K$ , $h_{fe}=50$ , $h_{re}=205 \times 10^{-4}$ , $h_{oe}=25 \mu A/V$ is connected in CE configuration as shown in fig. 	Evaluating	8
13	A common collector circuit has the following components $R_1=27k\Omega$ , $R_2=27k\Omega$ , $R_e=5.6k\Omega$ , $R_L=47k\Omega$ , $R_s=600\Omega$ . The transistor parameters are $h_{ie}=1k\Omega$ , $h_{fe}=85$ and $h_{oe}=2 \mu A/V$ . <b>Determine</b> $A_i$ , $R_i$ , $A_v$ , $R_o$ .	Evaluating	8
14	A common Emitter circuit has the following components. $R_s=1k$ , $R_1=110K$ , $R_2=12K$ , $R_c=6K$ . h-parameters are $h_{ie}=1.2K$ , $h_{re}=2.5 \times 10^{-4}$ , $h_{fe}=75$ , $h_{oe}=25 \mu A/V$ . <b>Draw</b> the equivalent hybrid model and calculate $A_i$ , $R_i$ , $R_o$ and $A_v$ ?		8
15	The h-parameters of a transistor used in a CE circuit are $h_{ie} = 1.0 K$ , $h_{re} = 10 \times 10^{-4}$ , $h_{fe} = 50$ , $h_{oe} = 100 K$ . The load resistance for the transistor is $1 K$ in the collector circuit. <b>Determine</b> $R_i$ , $R_o$ , $A_v$ & $A_i$ in the amplifier stage (Assume $R_s = 1000$ )?	Evaluating	8

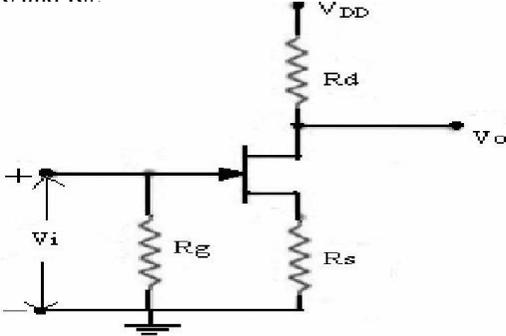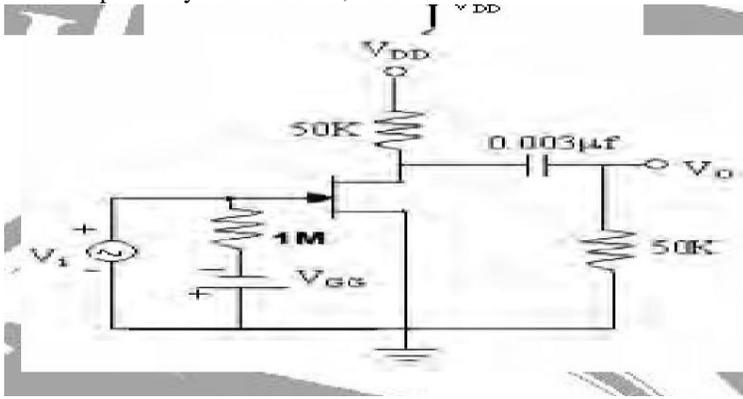S.No	QUESTION	Blooms taxonomy level	Course Outcomes
<b>UNIT-V</b> <b>FIELD EFFECT TRANSISTOR AND FET AMPLIFIERS</b>			
1	<p>A Common Source FET amplifier circuit shown in Figure.2 with un-bypassed <math>R_S</math> has the following circuit parameters: <math>R_d = 15K</math>, <math>R_S = 0.5K</math>, <math>R_g = 1M</math>, <math>r_d = 5K</math>, <math>g_m = 5mS</math> and <math>V_{DD} = 20 V</math>. Calculate <math>A_v</math>, <math>A_i</math>, <math>R_i</math> and <math>R_o</math>?</p> 		10
2	<p>In an n-channel FET, the effective channel width is <math>3x 10^{-4}cm</math> and the donor impurity concentration is <math>10^{15}</math> electrons/cm<sup>3</sup>. <b>Find</b> the pinch-off voltage?</p>	Evaluating	10
3	<p>In the common source FET amplifier shown in Figure.1, the trans conductance and drain dynamic resistance of the FET are <math>5mA/V</math> and <math>1M\Omega</math> respectively. <b>Estimate</b> <math>A_v</math>, <math>R_i</math> &amp; <math>R_o</math>?</p> 	Evaluating	10
4	<p>A Common Source FET amplifier circuit with un bypassed <math>R_S</math> has the following circuit parameters: <math>R_d = 15K</math>, <math>R_S = 0.5K</math>, <math>R_g = 1M</math>, <math>r_d = 5K</math>, <math>g_m = 5mS</math> and <math>V_{DD} = 20 V</math>. <b>Determine</b> <math>A_v</math> &amp; <math>R_o</math>?</p>	Evaluating	10
5	<p>A self biased p – channel JFET has a pinch – off voltage of <math>V_P = 5 V</math> and <math>I_{DSS} = 12 mA</math>. The supply voltage is <math>12 V</math>. <b>Determine</b> the values of <math>R_D</math> and <math>R_S</math> so that <math>I_D = 5 mA</math> and <math>V_{DS} = 6V</math>?</p>	Evaluating	10

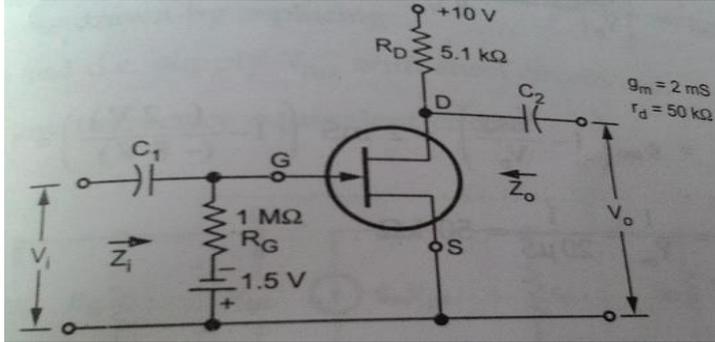S.No	QUESTION	Blooms taxonomy level	Course Outcomes
6	<p>For the circuit shown in fig. <b>Determine</b> i) Input impedance II) output impedance and III) voltage gain?</p> 	Evaluating	10
7	<p>The P-channel FET has a <math> I_{DS}  = -12\text{mA}</math>, <math> V_p  = 5\text{V}</math>, <math>V_{GS}</math> is 1.6 V. <b>Determine</b> <math>I_D</math>, <math>G_m</math> and <math>G_{m0}</math>?</p>	Evaluating	10
8	<p>Data sheet for a JFET indicates that <math>I_{DS} = 10\text{mA}</math> and <math>V_{GS(\text{off})} = -4\text{V}</math>. <b>Determine</b> the drain current for <math>V_{GS} = 0\text{V}</math>, <math>-1\text{V}</math> and <math>-4\text{V}</math>.</p>	Evaluating	10