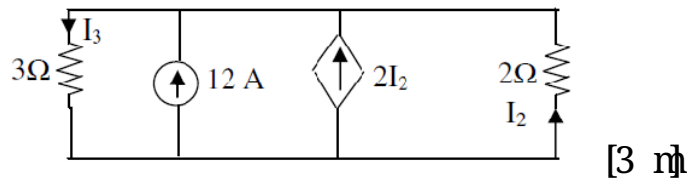


I I.TE c-hE C E NET WORK ANALYS IS QUEST I ON BANK

Un i1t


1. (a) Find the power delivered by each branch for



- (b) Explain the source transformation with a

2. (a) A resistor is connected across a capacitor which has been previously charged to a potential. If the potential difference is initially 500V and the resistance is 300Ω, the circuit

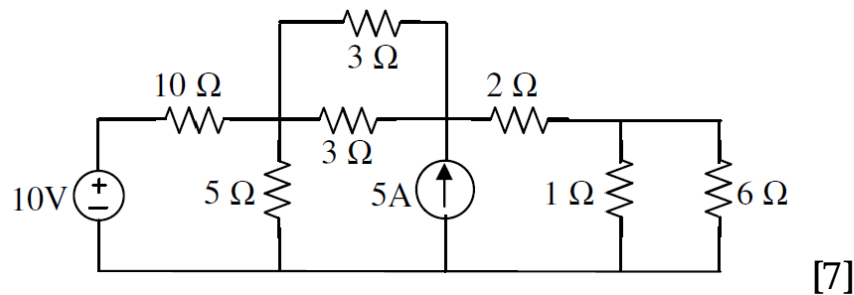- (b) Determine the voltage at each node of the




3. (a) Draw the graph corresponding to the following


$$A = \begin{bmatrix} -1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix} \quad [3]$$

(b) Explain the rms value and average value of a periodic waveform. Derive necessary expressions.

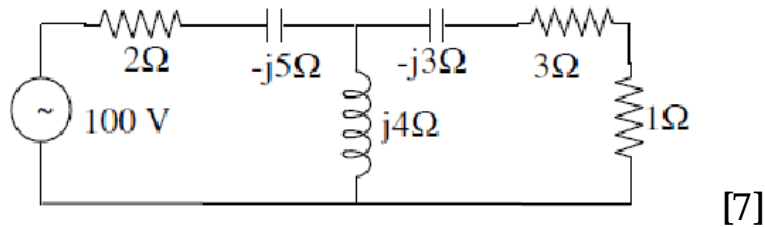4. (a) In the following network determine the average power supplied by the source and the average power absorbed by the resistor.



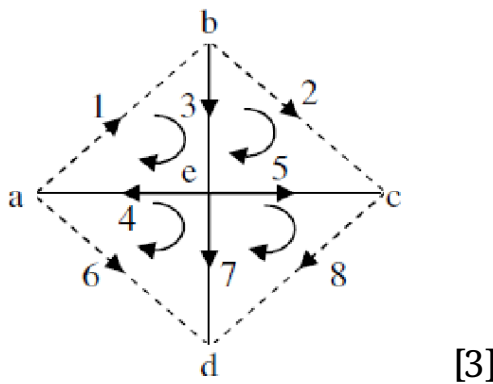(b) Write the fundamental matrix for the following graph.



5. (a) A series circuit has the voltage $v = 100 \sin(314t)$ and the current $i = 10 \cos(314t)$. Calculate the average power absorbed by the circuit.

. Find elements in the circuit
 (b) Determine form factor and peak factor of t

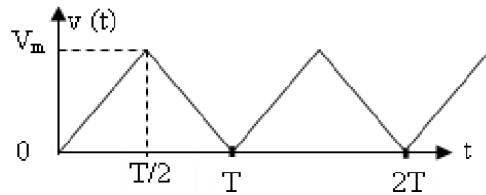


Figure 2

[7]

6. (a) Find the total power delivered in the circuit by the 125V source using the mesh current method


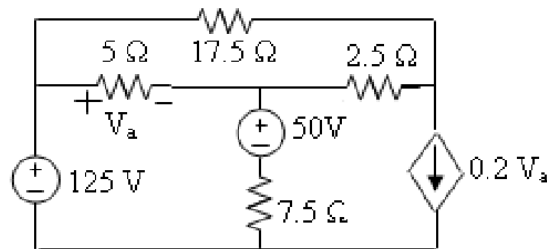


Figure 3

[7]

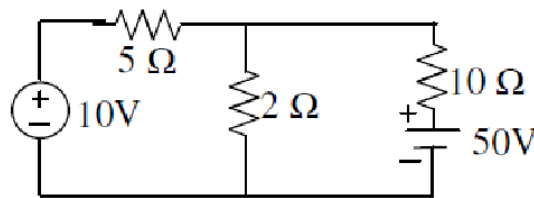
(b) Determine loop currents from the following circuit



[3]

7. (a) Define the following terms (i) form factor (ii) peak factor

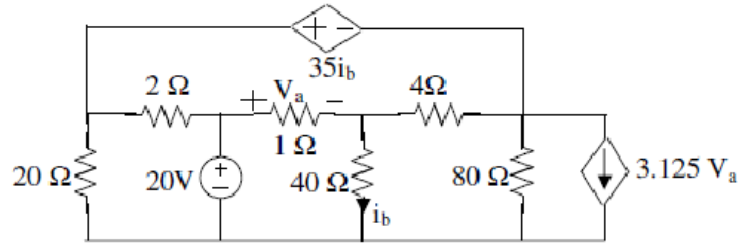(b) Use node voltage method to find the power delivered by the 10V source in the circuit from the following



[6]

Unit 2

1. (a) A coil of resistance r and inductance l is connected to a 50 Hz supply. The current through the coil is found to be 10 A and the power dissipated is 100 W.

Find r and l .

(b) Show that the real power consumed by a pure inductor is zero.

2. (a) A resistor r is connected in series with a combination of a capacitor C and an inductor l . This combination is connected to a 50 Hz AC supply. The voltage drop across the resistor is 60 V and the power dissipated in the resistor is 400 W.

(b) For an RC series circuit a voltage $v(t) = 100 \sin(314t)$ is applied at $t = 0$.

Find the expression for the transient current $i(t)$.

3. (a) A sinusoidal voltage $v(t) = 210 \sin(314t)$ is applied suddenly to a series combination of a resistor $r = 10 \Omega$ and an inductor $l = 0.01 H$.

RL circuit with $R=2\Omega$ and $L=2H$ find the instant at which current becomes zero

(b) The resistor r in series with capacitance $C=240\mu F$ supply the value of C so that r absorbs $100W$ and also the maximum charge

4. (a) A series circuit consists of 100Ω resistor and $0.318H$ and


A capacitor of unknown value is supplied by a $50V$ supply and draws a $3A$ current in the supply. find the value of the capacitor supplied by the source

(b) A series RLC circuit has $R=10\Omega$, $L=31.8\mu H$ and $C=1\mu F$ calculate the resonance frequency and calculate the voltage drops across R and C if the applied voltage is $100V$

5. (a) An R series circuit has $R=5\Omega$ and $L=1H$ find the power factor of the circuit if an alternating voltage is applied across the circuit

(b) A coil with a resistance of 7Ω and inductance $0.1H$ is connected to a $100V$ AC supply. find the current and power factor


6. Find value of voltage V_0 in the circuit shown in figure

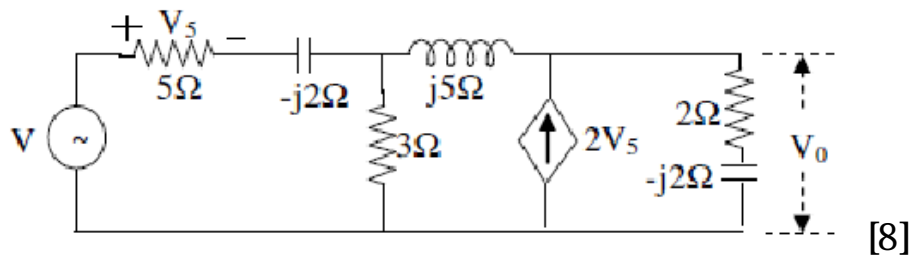

Unit 3

1. (a) Give a comparison between series and parallel circuits
 (b) A series RLC circuit consists of $R=10\Omega$, $L=31.8\mu H$ and $C=1\mu F$


- 0.4 h capacitance of 250 connected a supply of 250 V at 50 Hz. Find the total impedance, current, average power, average voltage across coil and capacitance
2. (a) Show that the resonant frequency is the geometric mean of the half power frequencies
 (b) Define self inductance and mutual inductance and its effect on coupling in a coupled circuit
 3. (a) Derive the expressions for quality factor in series RLC resonant circuit
 (b) Define quality factor. What is the significance of these parameters in series resonant circuit?
 4. (a) Two coupled coils have $L_1 = 10\text{ mH}$ and $L_2 = 20\text{ mH}$. The coefficient of coupling between them is 0.5. If a current $i = 10\cos(1000t)\text{ A}$ flows through coil 1, find the voltages across each coil and the induced EMF in coil 2.
 (b) An electrical circuit with $R = 10\ \Omega$, $L = 0.1\text{ H}$ and $C = 100\ \mu\text{F}$ are all connected in parallel. It is energized with a 50 Hz AC voltage. Calculate the current taken from the source, the power factor of the circuit and the real power.
 5. (a) What are the characteristics of parallel resonance?
 (b) For the circuit shown in figure, find the value of X_c for which the circuit is under resonance.

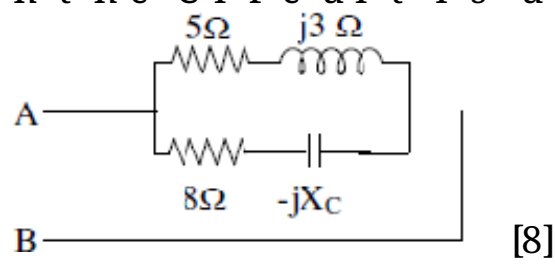


Unit 4

1. (a) State the theorem and maximum power transfer theorem.

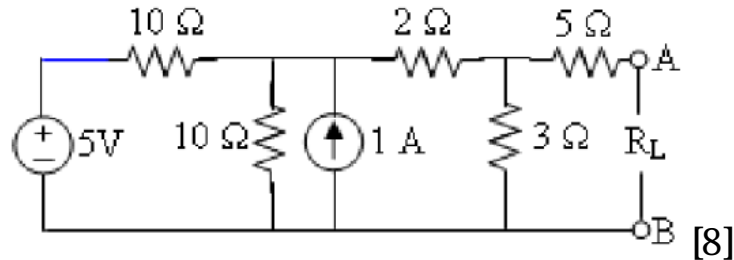(b) Find the resistance connected between the terminals so that maximum power is delivered to it. Determine the maximum power delivered following figure



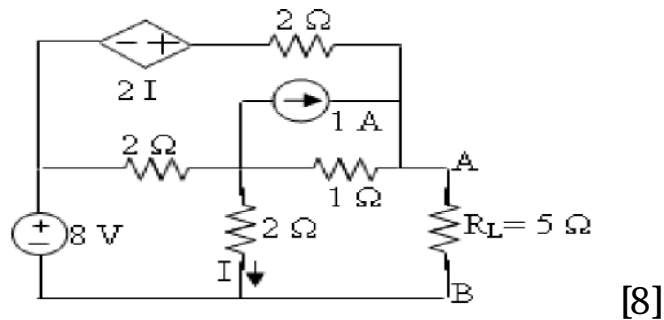2. (a) Determine the current through the load resistor following figure and also find maximum transferable power.



(b) State the limitations and write its applications.

3. (a) State maximum power transfer theorem and its limitations.

(b) Find the Norton's equivalent circuit.


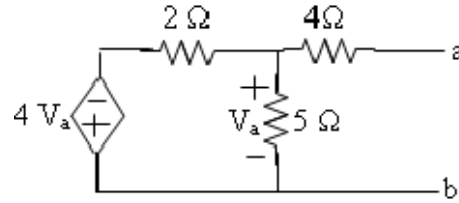


Figure 4

[8]

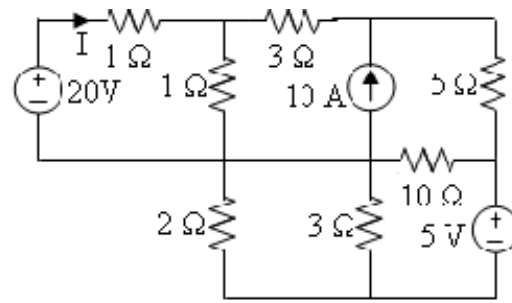4. (a) State reciprocity AND compensation THEOREM
 (b) Determine current i using superposition theorem



[8]

5. (a) Verify Thevenin theorem


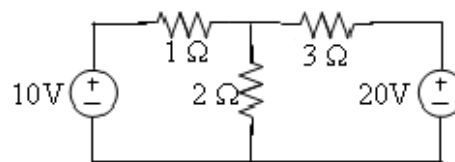


Figure 4


[5]

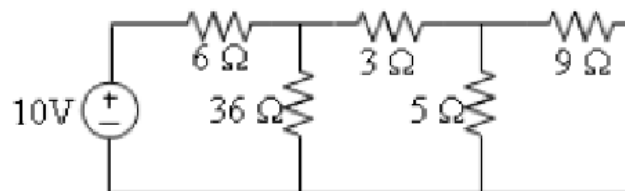- (b) Find currents i_1 and i_2 in the circuit from the circuit shown when the resistor is changing to compensation theorem




[5]

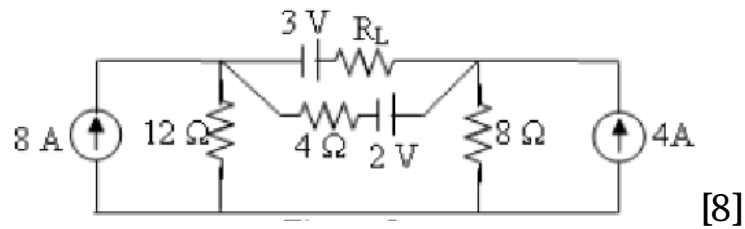6. Obtain the maximum amount of power that can be transferred to the load R_L in the following circuit using maximum power transfer theorem.



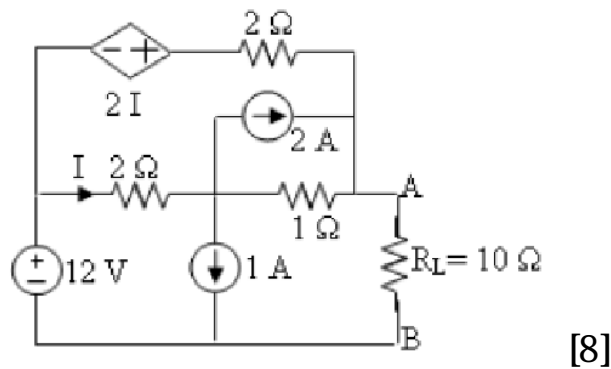
7. Determine the current I in the following circuit using thevenin's theorem and verify it by Norton's theorem.

for which maximum power will be transferred to the load R_L .




Unit-5

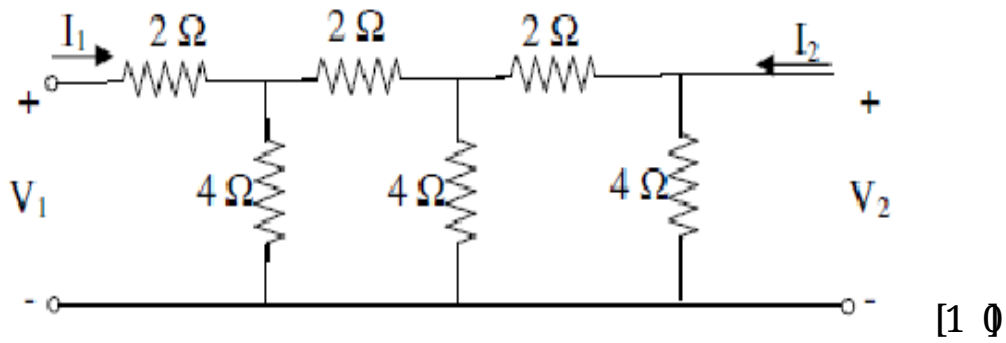1. (a) Prove the conditions for symmetry and reciprocity parameters [4]
- (b) Find a b c d parameters and transmission parameters of the following



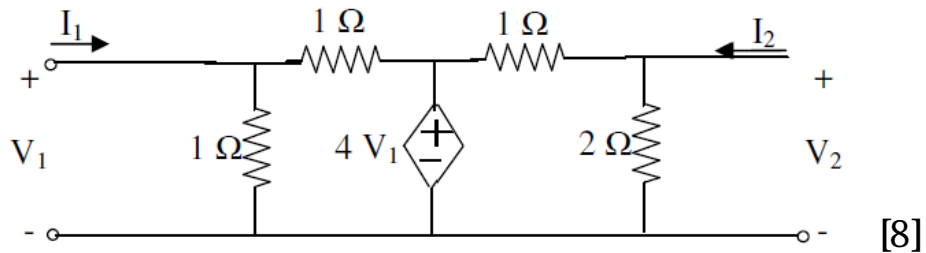2. (a) Derive Z parameters as function of h parameters [6]
- (b) Prove the conditions for symmetry and reciprocity transmission line parameters [4]
3. (a) Why Z-parameters are known as open circuit parameters and Y-parameters are known as short circuit parameters [4]
- (b) Derive H parameters as function of ABCD parameters [8]
4. (a) Determine Z parameters of the following circuit [8]



- (b) Prove the conditions for symmetry and reciprocity transmission parameters [4]

5. (a) The parameters of a network are
 $Z_{11} = 2 \Omega$, $Z_{22} = 4 \Omega$, $Z_{12} = Z_{21} = 1 \Omega$. Find ABCD parameters of this network.
 (b) Derive parameters in Y parameters.
6. Obtain the Admittance parameters of the network by obtaining parameters.

