

IV B.Tech II Semester Regular/Supplementary Examinations, July - 2021**HVDC TRANSMISSION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 70***Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any FOUR questions from Part-B*

PART-A(14 Marks)

1. a) State the merits of HVDC transmission over EHVAC transmission for bulk power transmission. [2]
- b) What are the five modes of region of rectifier operation of a 12-pulse converter? [2]
- c) Distinguish between delay in firing angle (α) and extinction angle (γ) of an HVDC converter. [3]
- d) List out the sources of reactive power in HVDC system. [2]
- e) What are the sources of generation of harmonics. [2]
- f) How is a filter designed? What are the different types of Ac filters. [3]

PART-B(4x14 = 56 Marks)

2. a) What are the different types of HVDC links? Discuss them with necessary diagrams. [6]
- b) With a neat schematic diagram, state the various apparatus required for HVDC station and explain the purpose of each. [8]
3. a) Obtain the relation between the DC output voltage and the AC line voltage(rms) and rating of converter transformer with Graetz's converter circuit [7]
- b) The AC line voltage is 330 kV with a load of 500MW and p.f =0.78 at the inverter end. Calculate the AC line voltage, current and p.f at the rectifier end with $\mu=15^\circ$. [7]
4. a) Explain the operation of a converter when working as an inverter, and state the necessary conditions required for inverter operation. [7]
- b) The DC voltage and current at the sending end of a rectifier station are 200 kV and 1000A respectively. The commutating reactance of the rectifier is 10 ohm and the resistance of the line is 10 ohm. Calculate the extinction angle γ , if the DC voltage is 190 kV at the terminal of the inverter. Assume the no load voltage of the inverter as 200 kV at $\gamma=0$. [7]
5. a) Describe the thyristor-controlled reactor with necessary diagrams and expressions. [5]
- b) Obtain the modelling of DC Links in HVDC system. [9]
6. a) Explain the development of DC circuit breaker. [9]
- b) What are the factors responsible for generation of characteristic and non-characteristic harmonics? How each can be reduced to a minimum? [5]
7. a) What are the different types of filters used on the AC side of an HVDC system? How are they located and arranged? [5]
- b) Describe the design of high pass filters. [9]